作业纸

班级:

姓名: **省沙印建** 学号: 1**820121053**

$$\begin{array}{lll}
9-2: \dot{U}_{m} = & (1020^{\circ} - 20230^{\circ}) \, V \\
&= & (10 - 17.32 - j10) \, V \\
&= & (-7.32 - j10) \, V \\
&= & 12.39 \, 2 - 126.2^{\circ} \, V \\
U = \frac{U_{m}}{\sqrt{32}} = \frac{12.39}{\sqrt{2}} \qquad P = \frac{U^{2}}{R} = \frac{76.78}{10} \\
&= 8.76 \, V \\
&= 7.68 \, W
\end{array}$$

$$9 - 10 : + \frac{Z_1}{Z_2}$$

$$(1) Z_2 // Z_3 = \frac{Z_1 Z_3}{Z_2 + Z_3}$$

$$5 / 53^\circ \times 5 / 90^\circ$$

$$= \frac{5.253^{\circ} \times 5.2-90^{\circ}}{5.253^{\circ} + 5.290^{\circ}}$$

$$= \frac{25.2-37^{\circ}}{3+34-35}$$

$$= \frac{20-315}{3-3}$$

$$= (7.5-32.5) \Omega$$

 $Z = 2_1 + 2_2 / 2_3$

$$(2) P = I^{2}R$$

$$= 10^{2} \times 8$$

$$= 800 W$$

$$R = \cos \theta_{2}$$

$$= \cos(-36.9^{\circ})$$

$$= 0.8$$

$$\dot{I} = \frac{100 \angle 90^{\circ}}{Z}$$

= 100 \(\tag{-90°}



作业纸

班级:

教学班级:

姓名:

学号:

第 页

$$Z = \frac{20(10+j100)}{20+(0+j100)}$$

$$=\frac{20+3200}{3+110}$$

$$= 10^2 \times 18.9$$

$$Q = I^2x$$

$$= 10^2 \times 3.67$$

$$S = \sqrt{p^2 + Q^2}$$

$$= \sqrt{1890^2 + 367^2}$$


$$Q_c = -wCV^2$$


$$C = -\frac{Q_c}{wV^2}$$

$$Q_c = -Q_c$$

应使
$$Q = Q_{\mathbb{R}} + Q_{\mathbb{C}} = C$$
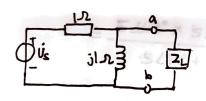
$$\therefore C = \frac{8}{100 \times (\frac{100}{\sqrt{2}})^2} = 10 \text{ MF}$$



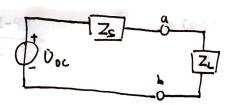

$$Z_s = \frac{jl}{l+jl}$$

$$P_{\text{Lmax}} = \frac{10^{\circ}}{4 \times 0.5}$$

$$= 50 \text{ W}$$

$$= (0.5 + j0.5) \Lambda$$

联系方式:_